

 


2.

 

4.

 

a) the flip-flop triggers on the negative edge of the clock pulse

b) the flip-flop triggers on the positive edge of the clock pulse

20)

1.  $t_{PLH}$  (clock to Q)

- time from triggering edge of clock to LOW-to-HIGH transition of the Q output.

2.  $t_{PHL}$  (clock to Q)

- time from triggering edge of clock to the HIGH-to-LOW transition of the Q output


3.  $t_{PLH}$  ( $\overline{PRE}$  to Q)

- time from triggering edge of clock to the HIGH-to-LOW transition of the Q output


4.  $t_{PHL}$  ( $\overline{CLR}$  to Q)

- time from assertion of the preset input to the LOW-to-HIGH transition of the Q output

22)

 


24)

 

$$T_{min} = 5ns + 2ns = 7ns$$

$$f_{max} = \frac{1}{T_{min}} = \frac{1}{7ns} = 142.9 MHz$$

25)

 

divide by 2

26)

