

Fibonacci sequence Circuit

PC/CP220 Project Phase III

Kevin Yejoon Lee

210872060

Fall 2022

Logic Equation

The equations for the outputs

$$B_3 = a_2 a_1 \neg a_0 + a_2 a_1 a_0$$

$$B_2 = a_2 \neg a_1 a_0 + a_2 a_1 a_0$$


$$B_1 = a_2 \neg a_1 \neg a_0 + \neg a_2 a_1 a_0$$

$$B_0 = \neg a_2 \neg a_1 a_0 + \neg a_2 a_1 \neg a_0 + a_2 \neg a_1 \neg a_0 + a_2 \neg a_1 a_0 + a_2 a_1 a_0$$

Circuit Diagram

Diagram of fibonacci converter

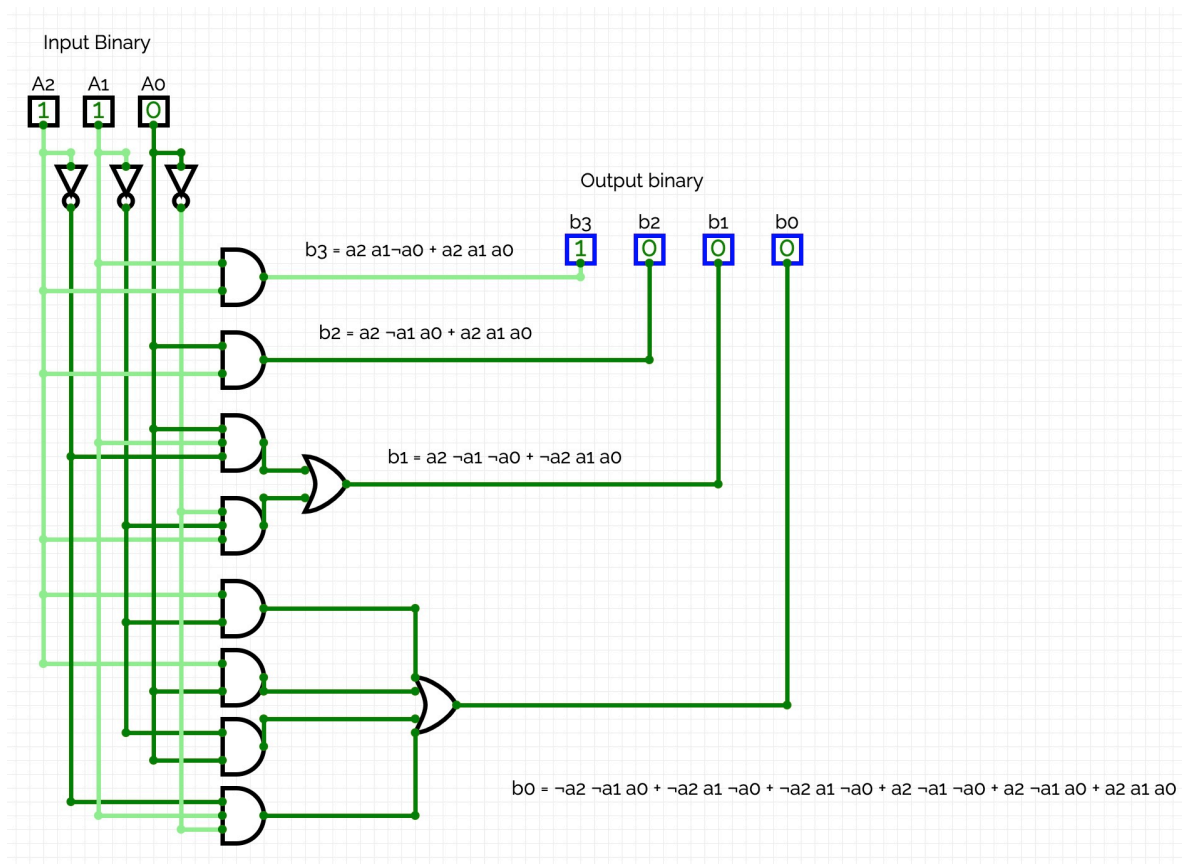The circuit was drawn using <https://circuitverse.org/> as shown in the following figure. Unlike other circuits, the output returns a binary number that represents the output fibonacci number rather than a boolean value like the prime identifier circuit. The circuit serves its purpose in finding the corresponding fibonacci number as proven in sections later on.



Circuit Outputs TT


All the circuit outputs = the expected fibonacci number

a_2	a_1	a_0	b_3	b_2	b_1	b_0
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	0	1	1
1	0	1	0	1	0	1
1	1	0	1	0	0	0
1	1	1	1	1	0	1

Therefore, the circuit serves its purpose in finding the corresponding fibonacci number.

Simulation Output

 All the circuit outputs = the expected fibonacci number



Parts List

List of all parts required to make circuit

In addition to the CPLD (Complex Programming Logic Device) we require,

- • DIP switch, for input
- • Resistor array for the DIP switch; probably $1k\Omega$ or so.
- • four LED (could use debugger board but LED's could demonstrate one bit each as well)
- • Resistor for the LED's; probably 510Ω or so each. (unless using debugger board)

Extra Proof for Circuit

There is a video with attached circuit demonstrating the working circuit outputs

END OF PROJECT PHASE 3

Check list attached below

PC/CP220 Project Phase III Checklist (3.01)

A. General

1. Professionally presented
Neat, etc. _____
2. Properly identified
(eg. name, id) _____
3. On time
at *beginning* of lab *with checklist* _____
4. Good grammar
(eg. complete sentences where required) _____
5. Correct spelling _____

B. Content

1. *Circuit diagram is
consistent with equations* _____
2. *All cases are simulated
with good explanations* _____
3. *Circuit passes/fails simulation
noted (matches truth table)* _____
4. *All input/output parts have been
listed (including resistors)* _____
5. *All previous phases included
(updated if necessary)* _____

Fibonacci sequence Circuit

PC/CP220 Project Phase II

Kevin Yejoon Lee

210872060

Fall 2022


Table of Contents

Table of Contents.....
TT containing only binary quantities.....
K - maps
Output b3.....
Output b2.....
Output b1.....
Output b0.....
Equation Testing/SOP
Summary
Project Phase II Checklist.....
 Description.....
Inputs.....
Outputs.....
Identical Output case.....
Final Truth Table.....
Project Phase I Checklist.....


TT containing only binary quantities

Each bit to be broken down into a k-map


a_2	a_1	a_0	b_3	b_2	b_1	b_0
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	0	1	1
1	0	1	0	1	0	1
1	1	0	1	0	0	0
1	1	1	1	1	0	1

 


$$AB\bar{C} + ABC$$

 

$$A\bar{B}\bar{C} + ABC$$

 

$$A\bar{B}\bar{C} + \bar{A}BC$$

 

$$A\bar{B} + AC + \bar{B}C + \bar{A}\bar{B}\bar{C}$$

SOP Formulas

Solutions to SOP

Outputs	Solution	SOP
b_3	AB	$AB\bar{C} + ABC$
b_2	AC	$A\bar{B}C + ABC$
b_1	$A\bar{B}\bar{C} + \bar{A}BC$	$A\bar{B}\bar{C} + \bar{A}BC$
b_0	$A\bar{B} + AC + \bar{B}C + \bar{A}B\bar{C}$	$\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$

Equation Testing

Each output tested in maxima

b_3	<pre> %i1) f:(a and b and not c) or (a and b and c); (%o1) a∧b∧¬c∨a∧b∧c %i2) f, a=true, b=true ,c=true; (%o2) true %i3) f, a=true, b=true ,c=false; (%o3) true %i4) f, a=true, b=false ,c=true; (%o4) false %i5) f, a=true, b=false ,c=false;</pre>
-------	---

	(%o5) false
	(%i6) f, a=false, b=true ,c=true; (%o6) false
	(%i7) f, a=false, b=true ,c=false; (%o7) false
	(%i8) f, a=false, b=false ,c=true; (%o8) false
	(%i9) f, a=false, b=false ,c=false; (%o9) false

b₂

(%i1)
f:(a and not b and c) or (a and b and c);
(%o1) $a \wedge \neg b \wedge c \vee a \wedge b \wedge c$

(%i2)
f, a=true, b=true ,c=true;
(%o2) true

(%i3)
f, a=true, b=true ,c=false;
(%o3) false

(%i4)
f, a=true, b=false ,c=true;
(%o4) true

(%i5)
f, a=true, b=false ,c=false;
(%o5) false

(%i6)
f, a=false, b=true ,c=true;
(%o6) false

(%i7)
f, a=false, b=true ,c=false;
(%o7) false

(%i8)
f, a=false, b=false ,c=true;
(%o8) false

(%i9)
f, a=false, b=false ,c=false;
(%o9) false

b₁	<pre>(%i1) f:(a and not b and not c) or (not a and b and c); (%o1) a∧¬b∧¬c∨¬a∧b∧c (%i2) f, a=true, b=true ,c=true; (%o2) false (%i3) f, a=true, b=true ,c=false; (%o3) false (%i4) f, a=true, b=false ,c=true; (%o4) false (%i5) f, a=true, b=false ,c=false; (%o5) true (%i6) f, a=false, b=true ,c=true; (%o6) true (%i7) f, a=false, b=true ,c=false; (%o7) false (%i8) f, a=false, b=false ,c=true; (%o8) false (%i9) f, a=false, b=false ,c=false; (%o9) false</pre>
b₀	<pre>(%i1) f:(not a and not b and c) or (not a and b and not c) or (a and not b and not c) or (a and not b and c) or (a and b and c); (%o1) ¬a∧¬b∧c∨¬a∧b∧¬c∨a∧¬b∧¬c∨a∧¬b∧c∨a∧b∧c (%i2)</pre>

Summary

The equations for the outputs are

$$B_3 = a_2 a_1 \neg a_0 + a_2 a_1 a_0$$

$$B_2 = a_2 \neg a_1 a_0 + a_2 a_1 a_0$$

$$B_1 = a_2 \neg a_1 \neg a_0 + \neg a_2 a_1 a_0$$

$$B_0 = \neg a_2 \neg a_1 a_0 + \neg a_2 a_1 \neg a_0 + a_2 \neg a_1 \neg a_0 + a_2 \neg a_1 a_0 + a_2 a_1 a_0$$

f, a=true, b=true ,c=true;
(%o2) true

(%i3)

f, a=true, b=true ,c=false;
(%o3) false

(%i4)

f, a=true, b=false ,c=true;
(%o4) true

(%i5)

f, a=true, b=false ,c=false;
(%o5) true

(%i6)

f, a=false, b=true ,c=true;
(%o6) false

(%i7)

f, a=false, b=true ,c=false;
(%o7) true

(%i8)

f, a=false, b=false ,c=true;
(%o8) true

(%i9)

f, a=false, b=false ,c=false;
(%o9) false

PC/CP220 Project Phase II Checklist (3.01)

A. General

1. Professionally presented
Neat, etc. _____
2. Properly identified
(eg. name, id) _____
3. On time
at *beginning* of lab *with checklist* _____
4. Good grammar
(eg. complete sentences where required) _____
5. Correct spelling _____

B. Content

1. *All outputs analyzed*
(truth table) _____
2. *Karnaugh maps (or equations)*
match truth table _____
3. *Equations tested*
(Maple, Maxima, etc.) _____
4. *Summary statement*
(all equations pass all tests) _____
5. *Previous phase included*
(updated if necessary) _____

Fibonacci sequence Circuit

PC/CP220 Project Phase I


Kevin Yejoon Lee

210872060

Fall 2022

Description

 They are specific numbers that we see in nature all the time, sometimes called *nature's code*. Together they are called the Fibonacci sequence.



The idea is simple: the next number is equal to the last two numbers in the sequence. If you look in nature these numbers appear everywhere. Bananas will contain three seed sections, apples five, in fact, chances are that no matter the plant you are looking at it will have 3,5,8,13 ~ pedals or seeds sections. (pine cones, snail shells, broccoli, pineapples, etc)

In nature these numbers represent the most efficient way to pack as many seeds as possible.

Inputs

The **Fibonacci sequence Circuit** will have 3 inputs, a_0 to a_2 which represent the binary representation of the number to be indexed from the fibonacci sequence. The input representing 1 will represent the first number in the sequence. The maximum decimal number these bits can represent is 7.

Outputs

The **Fibonacci sequence Circuit** will have 4 outputs b_0 to b_3 which represent the binary presentation of the number outputted at that index, the index of 3 will give an output of 2 according to the sequence. The maximum decimal number these bits can represent is 15.

Identical Output case

Table below shows two cases where output is identical

Input Decimal	$a_2 a_1 a_0$	Output	$b_3 b_2 b_1 b_0$
1	001	1	0001
2	010	1	0001

Final Truth Table

Table below gives a summary of the circuit's behavior.

Input Decimal	$a_2 a_1 a_0$	Output	$b_3 b_2 b_1 b_0$
0	000	0	0000
1	001	1	0001
2	010	1	0001
3	011	2	0010
4	100	3	0011
5	101	5	0101
6	110	8	1000
7	111	13	1101

PC/CP220 Project Phase I Checklist (3.01)

A. General

1. Professionally presented
Neat, etc. _____
2. Properly identified
(eg. name, id) _____
3. On time
at *beginning* of lab *with checklist* _____
4. Good grammar
(eg. complete sentences where required) _____
5. Correct spelling _____

B. Content

1. *Sufficient background*
(ie. problem circuit is to solve) _____
2. *Inputs are specified*
(eg. A_0, A_1, A_2, A_3 - binary) _____
3. *Outputs are specified*
(eg. L_1, S_1, L_2, S_2 , etc. - dashes/dots) _____
4. *Error conditions and responses*
to them are specified
(or stated that none exist) _____
5. *Ambiguous possibilities have been*
eliminated (ie. don't care conditions)
(or stated that none exist) _____